

3-(a) For natural angular frequency  $\omega_0$ ,

$$Lq'' + \frac{q}{C} = E_0 \sin(\omega_0 t) \quad \text{when } E_0 = 0$$

So  $Lq'' + \frac{q}{C} = 0$  Let's multiply both sides with C. LC  $q'' + q = 0$ . Let's assume  $q = e^{kt}$ . LC  $q'' + q = (LCk^2 + 1)e^{kt} = 0$  since  $e^{kt} \neq 0$ .  $LCk^2 + 1 = 0$  thus  $k = \pm \frac{1}{\sqrt{LC}}i$  making  $q(t) = e^{\pm \frac{1}{\sqrt{LC}}it}$

$$\tilde{q}(t) = e^{\pm \frac{1}{\sqrt{LC}}it} = \cos(\frac{1}{\sqrt{LC}}t) \pm i \sin(\frac{1}{\sqrt{LC}}t) \quad \text{thus } q(t) = A \sin(\frac{1}{\sqrt{LC}}t) + B \cos(\frac{1}{\sqrt{LC}}t) \quad \text{where } A, B \text{ are constants. Thus we can see that } \omega_0 = \frac{1}{\sqrt{LC}}.$$

3-(b) When  $E_0 \neq 0$ ,  $\omega \neq \omega_0$

$$Lq'' + \frac{q}{C} = E_0 \sin(\omega t)$$

We found out at 3-(a) that  $q(t) = A \sin(\frac{1}{\sqrt{LC}}t) + B \cos(\frac{1}{\sqrt{LC}}t)$ . Now for  $q''L + \frac{q}{C} = E_0 \sin(\omega t)$ , let's assume  $q(t) = D \sin \omega t + E \cos \omega t$ . (D, E are constants)

$$\text{Then } q''L + \frac{q}{C} = L\omega^2(-D \sin \omega t - E \cos \omega t) + \frac{1}{C}(D \sin \omega t + E \cos \omega t)$$

$$= \sin \omega t (-L\omega^2 D + \frac{1}{C}D) + \cos \omega t (-L\omega^2 E + \frac{1}{C}E) = E_0 \sin \omega t. \quad \text{Since } \omega \neq \omega_0, E = 0. \text{ Making } E_0 \sin \omega t = D(-L\omega^2 + \frac{1}{C}) \sin \omega t.$$

$$E_0 = D(-L\omega^2 + \frac{1}{C}) \Rightarrow D = \frac{E_0}{-L\omega^2 + \frac{1}{C}} = -\frac{E_0}{L} \cdot \frac{1}{\omega^2 - \omega_0^2}$$

$$\text{thus } q(t) = -\frac{E_0}{L} \cdot \frac{1}{\omega^2 - \omega_0^2} \cdot \sin \omega t \quad \text{therefore } q(t) = q_p(t) + q_h(t) = -\frac{E_0}{L} \cdot \frac{1}{\omega^2 - \omega_0^2} \cdot \sin \omega t + A \sin \omega_0 t + B \cos \omega_0 t$$

$$q'(t) = -\frac{E_0 \omega}{L} \cdot \frac{1}{\omega^2 - \omega_0^2} \cdot \cos \omega t + A \omega_0 \cos \omega_0 t - B \omega_0 \sin \omega_0 t$$

$$\Rightarrow q(0) = B, \quad q'(0) = \frac{E_0 \omega}{L} \cdot \frac{1}{\omega_0^2 - \omega^2} + A \omega_0$$

$$\Rightarrow A = \frac{1}{\omega_0} \left( q'(0) - \frac{E_0 \omega}{L} \cdot \frac{1}{\omega_0^2 - \omega^2} \right)$$

$$\therefore q(t) = -\frac{E_0}{L} \cdot \frac{1}{\omega^2 - \omega_0^2} \cdot \sin \omega t + \frac{1}{\omega_0} \left( q'(0) - \frac{E_0 \omega}{L} \cdot \frac{1}{\omega_0^2 - \omega^2} \right) \sin \omega_0 t + q(0) \cos \omega_0 t$$

3-(c)  $E_0 \neq 0$ ,  $\omega = \omega_0$ ,  $q_h(t) = q_p(t) = 0$ .

We solved from above that  $q(t) = A \cos \omega t + B \sin \omega t$  (A, B are constants)

$$\text{When } Lq'' + \frac{q}{C} = E_0 \sin \omega t \quad q(t) = Et \cos \omega t + Ft \sin \omega t \quad (F, E \text{ are constants})$$

$$q'(t) = E(\cos \omega t - \omega t \sin \omega t) + F(\sin \omega t + \omega t \cos \omega t)$$

$$q''(t) = E(-2\omega t \sin \omega t - \omega^2 t \cos \omega t) + F(2\omega t \cos \omega t - \omega^2 t \sin \omega t)$$

$$\text{So } Lq'' + \frac{q}{C} = \sin \omega t \left( -2E\omega_0 L - F\omega_0^2 L t + \frac{1}{C} \cdot Ft \right)$$

$$+ \cos \omega t (2F\omega_0 L - E\omega_0^2 L t + \frac{1}{C} \cdot Et)$$

$$= E_0 \sin \omega t$$

$$\Rightarrow \begin{cases} 2F\omega_0 L + Et(\frac{1}{C} - \omega_0^2 L) = 0 \\ -2E\omega_0 L + Ft(\frac{1}{C} - \omega_0^2 L) = E_0 \end{cases} \quad \text{as } \frac{1}{C} - \omega_0^2 L = \frac{1}{C} - \frac{1}{C} = 0 \quad \text{thus } 2F\omega_0 L = 0 \quad \text{and } -2E\omega_0 L = E_0 \quad \therefore F = 0, E = -\frac{E_0}{2\omega_0 L}$$

$$\text{Hence, } q(t) = A \cos \omega t + B \sin \omega t - \frac{E_0}{2\omega_0 L} t \cos \omega t. \quad q(0) = A = 0$$

$$q'(t) = -A\omega_0 \sin \omega t + B\omega_0 \cos \omega t - \frac{E_0}{2\omega_0 L} (\cos \omega t - \omega t \sin \omega t). \quad q'(0) = B\omega_0 - \frac{E_0}{2\omega_0 L} = 0 \Rightarrow B = \frac{E_0}{2\omega_0^2 L}$$

$$\therefore q(t) = \frac{E_0}{2\omega_0^2 L} \sin \omega t - \frac{E_0}{2\omega_0 L} t \cos \omega t$$

the charges does not decay and the amplitude increases



3 - (d)

$$\text{Now } L \cdot q'' + R \cdot q' + \frac{1}{C} q = \mathcal{E}_0.$$

Let's first assume the particular solution.

$$\vec{q}_{\text{part}} = A, \text{ then } L \cdot q'' + R \cdot q' + \frac{1}{C} q = \frac{A}{C} = \mathcal{E}_0 \Rightarrow A = C \cdot \mathcal{E}_0. \text{ hence } q_{\text{part}} = C \cdot \mathcal{E}_0.$$

$$\text{Now let's get the homogeneous solution. } L \cdot q'' + R \cdot q' + \frac{1}{C} q = 0. \text{ Assume } \vec{q}_{\text{hom}} = e^{kt}, \text{ then } e^{kt} (Lk^2 + Rk + \frac{1}{C}) = 0.$$

As  $e^{kt} > 0$ ,  $Lk^2 + Rk + \frac{1}{C} = 0$  has to be satisfied. Depending on  $R$  we can divide the general solution into three cases.

$$1) R^2 > \frac{4L}{C}, \text{ then } k = \frac{-R \pm \sqrt{R^2 - \frac{4L}{C}}}{2L} \text{ as } R^2 - \frac{4L}{C} > 0, q(t) = A \cdot e^{\frac{-R + \sqrt{R^2 - \frac{4L}{C}}}{2L} t} + B \cdot e^{\frac{-R - \sqrt{R^2 - \frac{4L}{C}}}{2L} t} + C \cdot \mathcal{E}_0.$$

$$2) R^2 = \frac{4L}{C}, \text{ then } k = \frac{-R}{2L} \text{ thus } q_{\text{hom}}(t) = C \cdot e^{-\frac{R}{2L} t} + D \cdot t \cdot e^{-\frac{R}{2L} t} \text{ making } q(t) = C \cdot e^{-\frac{R}{2L} t} + D \cdot t \cdot e^{-\frac{R}{2L} t} + C \cdot \mathcal{E}_0.$$

$$3) R^2 < \frac{4L}{C}, \text{ then } k = \frac{-R \pm \sqrt{R^2 - \frac{4L}{C}}}{2L} \text{ but as } R^2 - \frac{4L}{C} < 0 \Rightarrow k = \frac{-R \pm i \sqrt{\frac{4L}{C} - R^2}}{2L} \text{ (i = } \sqrt{-1} \text{). which makes } q_{\text{hom}} = e^{-\frac{R}{2L} t} \cdot \left( E \cdot \cos\left(\frac{\sqrt{\frac{4L}{C} - R^2}}{2L} t\right) + F \cdot \sin\left(\frac{\sqrt{\frac{4L}{C} - R^2}}{2L} t\right) \right) + C \mathcal{E}_0.$$

We can see that  $q(t)$  oscillates only when  $R^2 < \frac{4L}{C}$ .

$\therefore$  Hence if  $R^2 \geq \frac{4L}{C}$  is satisfied the current will not oscillate. This is true as  $I_{\text{current}} = \frac{dq}{dt}$ .